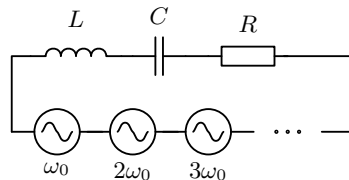


**Problem V.5 ... tuning a circuit**

9 points; průměr 1,64; řešilo 22 studentů

Consider a series circuit with a resistor of resistance  $R$ , a coil, and a capacitor with the capacitance  $C$ . AC voltage sources with identical amplitudes  $U$  are connected in series with these components. These sources vary in frequency by being multiples of  $\omega_0$ , where  $n$  represents an integer. What frequency, denoted by  $\omega_0$ , would allow us to find a coil possessing an inductance  $L$ , such that voltages with frequencies different from  $N\omega_0$  are suppressed by at least 90% on the resistor?  $N$  is a positive natural number known in advance (i.e., the value of  $\omega_0$  may depend on it), and we do not want to suppress the voltage with frequency  $N\omega_0$  by more than 90%.



*Jarda wanted to have as many different sources in the circuit as possible.*

Let's take a look at a simpler situation first. For the voltage across a resistor in a series RLC circuit with an impedance  $z_n$  and a voltage source of  $U_n = U \sin(n\omega_0 t)$  the following applies

$$U_R = IR = \frac{U}{|z|} R = \frac{R}{\sqrt{R^2 + \left(n\omega_0 L - \frac{1}{n\omega_0 C}\right)^2}} U.$$

If we want the voltage on this resistor to be damped by at least 90%, then it must hold  $U_R \leq \alpha U$  for  $\alpha = 0.1$ .

If we now connect more sources to the circuit as stated in the task, their superposition will give the total voltage. However, the linear behavior of the RLC circuit implies that we can solve for the voltages of different frequencies separately – for each one, we calculate the impedance, and according to the relation above we derive the partial voltage across the resistor.

The condition from the specification then states that, for all  $n \neq N$ , must hold

$$\frac{R}{\sqrt{R^2 + \left(n\omega_0 L - \frac{1}{n\omega_0 C}\right)^2}} \leq \alpha \quad (1)$$

and at the same time

$$\frac{R}{\sqrt{R^2 + \left(N\omega_0 L - \frac{1}{N\omega_0 C}\right)^2}} > \alpha. \quad (2)$$

Let  $n \neq N$  and let us solve the inequality (1):

$$\begin{aligned} \left(\frac{R}{\alpha}\right)^2 &\leq R^2 + \left(n\omega_0 L - \frac{1}{n\omega_0 C}\right)^2, \\ R\sqrt{\frac{1}{\alpha^2} - 1} &\leq \left|n\omega_0 L - \frac{1}{n\omega_0 C}\right|, \end{aligned} \quad (3)$$

from where

$$L \in \mathbb{R}^+ \setminus \left( \frac{1}{n^2 \omega_0^2 C} - \frac{A}{n\omega_0}, \frac{1}{n^2 \omega_0^2 C} + \frac{A}{n\omega_0} \right),$$

where  $A = R\sqrt{1/\alpha^2 - 1}$  a  $n \neq N$ ; for the sake of correctness, let us also mention that by the set  $\mathbb{R}^+$  we do not formally mean the set of positive real numbers, but the set of admissible values

of coil inductances (the difference is in the unit). By analogy, we also solve the equation (2), where we get

$$L \in \left( \frac{1}{N^2\omega_0^2 C} - \frac{A}{N\omega_0}, \frac{1}{N^2\omega_0^2 C} + \frac{A}{N\omega_0} \right).$$

If for  $n \in \mathbb{N}$  we denote

$$l_n = \frac{1}{n^2\omega_0^2 C} - \frac{A}{n\omega_0},$$

$$p_n = \frac{1}{n^2\omega_0^2 C} + \frac{A}{n\omega_0},$$

and  $J_n = (l_n, p_n)$  interval with these extreme points, we can rewrite the condition from the problem as

$$L \in [\mathbb{R}^+ \cap J_N] \setminus \bigcup_{\substack{n \in \mathbb{N} \\ n \neq N}} J_n.$$

This can be interpreted to mean that in the system of intervals  $J_n$  with the edge points  $l_n$  and  $p_n$  under study, we find when  $J_N$  contains a positive value  $L$  that is not also contained in any of the  $J_n$  intervals for  $n \neq N$ .

We will now claim that we can find a satisfying  $L$  precisely when  $p_{N+1} < l_{N-1}$ . To this end, we will make several observations.

1. The sequence  $p_n$  consists of positive numbers and decreases monotonically to zero.
2. The sequence  $l_n$  also converges to zero, and apparently from some  $n_0$  its terms will always be negative.
3. If  $\omega_0$  is such that  $l_{N-1} \leq 0$ , then necessarily (because of the monotonicity of  $p_n$ ) will hold

$$\mathbb{R}^+ \cap (l_{N-1}, p_{N-1}) \supseteq \mathbb{R}^+ \cap (l_N, p_N),$$

therefore the condition of the assignment cannot be fulfilled. Therefore, we will be interested in such frequencies  $\omega_0$  where  $l_{N-1} > 0$ .

4. Let us see when the sequence  $l_n$  is monotonic. After a continuous extension of the defining domain<sup>1</sup>, we can write

$$0 > \frac{dl_n}{dn} = \frac{1}{n^2\omega_0} \left( A - \frac{2}{n\omega_0} \right) \iff n < \frac{2}{\omega_0 C A},$$

which is specially fulfilled if  $l_{n+1} > 0$ . For this reason, the sequence  $l_n$  is decreasing as long as its values are positive.

5. If  $p_{N+1} < l_{N-1}$ , then an interval  $(p_{N+1}, l_{N-1})$  has a non-empty intersection with interval  $J_N$ . In this intersection we can choose  $L$ , this will then be an element of the interval  $J_N$ , but since  $L > p_{N+1} > p_{N+2} > \dots$ , it will not be an element of intervals  $J_{N+1}$ ,  $J_{N+2}$  nor the following. Likewise  $0 < L < l_{N-1} < l_{N-2} < \dots < l_1$ , is therefore not even an element of intervals  $J_1$  to  $J_{N-1}$ .

---

<sup>1</sup>so that we can derive

6. If, on the other hand,  $p_{N+1} \geq l_{N-1}$ , we also have  $l_{N+1} < l_N < l_{N-1} \leq p_{N+1} < p_N < p_{N-1}$ , and so

$$J_N \subseteq J_{N-1} \cap J_{N+1},$$

therefore the condition of the assignment cannot be fulfilled.

Thanks to all of the above, we know that it must hold  $p_{N+1} < l_{N-1}$ , let us write

$$\begin{aligned} \frac{1}{(N+1)^2\omega_0^2 C} + \frac{A}{(N+1)\omega_0} &< \frac{1}{(N-1)^2\omega_0^2 C} - \frac{A}{(N-1)\omega_0}, \\ \omega_0 A \left( \frac{1}{N+1} + \frac{1}{N-1} \right) &< \frac{1}{C} \left( \frac{1}{(N-1)^2} - \frac{1}{(N+1)^2} \right), \\ \omega_0 &< \frac{2}{AC} \frac{1}{N^2 - 1}, \end{aligned}$$

which is a required condition.

To the extent that the above solution is rather mathematical, we will give some more physical intuition. The RLC circuit has its resonant frequency and the more the source frequency differs from this resonant frequency, the more damped it will be. Therefore, it is sufficient to check only the damping of two adjacent frequencies – because if we damp them sufficiently, voltages with frequencies even further away from the resonant frequency of the circuit will be damped even more (this is exactly the monotonicity we mentioned several times above). The value of  $L$  will therefore be chosen so that the resonant frequency  $\omega_r = 1/\sqrt{LC}$  was close  $N\omega_0$ . A more physical approach, where we assume a known shape of the resonance curve, could then look like this: The attenuation of an RLC circuit according to a given frequency is expressed by a resonance curve that has one maximum at the resonant frequency, the width of which is determined by the circuit parameters. The width of the curve at point 90% attenuation can be expressed from the equation (3). With the use of substitution  $A = R\sqrt{1/\alpha^2 - 1}$  we get, for extreme points, considering only positive frequencies

$$\begin{aligned} \omega_1 &= \frac{-AC + \sqrt{A^2 C^2 + 4LC}}{2LC}, \\ \omega_2 &= \frac{AC + \sqrt{A^2 C^2 + 4LC}}{2LC}. \end{aligned}$$

The distance between them  $\Delta\omega = A/L$  then must be less than  $2\omega_0$ , so that in an interval with an attenuation of less than 90% was only the frequency  $N\omega_0$  and not the frequency of other sources. From this, we conclude that we are looking for a limit to  $\omega_0$ , when the adjacent frequency  $(N-1)\omega_0$  and  $(N+1)\omega_0$  are just the cutoff frequencies  $\omega_1$  and  $\omega_2$ . Target frequency  $N\omega_0$  in this case will be exactly in the middle of the interval, i.e. the average  $\omega_1$  and  $\omega_2$

$$N\omega_0 = \frac{\omega_1 + \omega_2}{2} = \frac{\sqrt{A^2 + C^2 + 4LC}}{2LC} = \sqrt{\frac{A^2}{4L^2} + \frac{1}{LC}}.$$

From this relation, we now express the appropriate inductance (choose a positive result)

$$\begin{aligned} 0 &= 4L^2 C N^2 \omega_0^2 - 4L - A^2 C, \\ L &= \frac{1 + \sqrt{1 + A^2 C^2 N^2 \omega_0^2}}{2N^2 \omega_0^2 C}. \end{aligned}$$

By setting the inductance to a condition  $\Delta\omega < 2\omega_0$  we get

$$2\omega_0 > \frac{A}{L} = \frac{2N^2\omega_0^2 CA}{1 + \sqrt{1 + A^2 C^2 N^2 \omega_0^2}},$$

$$\sqrt{1 + A^2 C^2 N^2 \omega_0^2} > N^2 \omega_0 CA - 1,$$

$$1 + A^2 C^2 N^2 \omega_0^2 > N^4 \omega_0^2 C^2 A^2 - 2N^2 \omega_0 CA + 1,$$

$$AC(1 - N^2)\omega_0 > -2,$$

$$\omega_0 < \frac{2}{AC} \frac{1}{N^2 - 1}.$$

So we get the same result as in the previous procedure.

**Vojtěch David**  
vojtech.david@fykos.org

**Kateřina Rosická**  
kacka@fykos.org

---

FYKOS is organized by students of Faculty of Mathematics and Physics of Charles University. It's part of Media Communications and PR Office and is supported by Institute of Theoretical Physics of MFF UK, his employees and The Union of Czech Mathematicians and Physicists. The realization of this project was supported by Ministry of Education, Youth and Sports of the Czech Republic.

This work is licensed under Creative Commons Attribution-Share Alike 3.0 Unported. To view a copy of the license, visit <https://creativecommons.org/licenses/by-sa/3.0/>.